

# SAWTOOTH SUBOCTAVE GENERATOR

CMOS circuits powered from +/-5V rails  
(74xx circuits not suitable, even if CMOS versions)

a logic high level (+5V) on RESET will  
force the output into its first half-period  
(similar to soft sync)

